



# Verilog HDL

---

Presented by: Amir Masoud Gharehbaghi

Email: [amgh@mehr.sharif.edu](mailto:amgh@mehr.sharif.edu)



# Design Hierarchy

---

Design Specification & Requirements



Behavioral Design



Register Transfer Level (RTL) Design



Logic Design



Circuit Design



Physical Design



Manufacturing



# Design Automation (DA)

---

- Automatic doing task in design process:
  - Transforming one form of design to another
  - Verifying functionality and timing of design
  - Generating test sequence for design validation
  - Documentation
  - ...




# Hardware Description Languages (HDLs)


---

Describing Hardware for:

 - Design & Modeling
- Simulation
- Synthesis
- Testing
- Documentation
- ...



# Top-Down Design

 



# Verilog General Features

---


- Support for timing information
- Support for concurrency


 
# Verilog Abstraction Models

---

- Algorithmic
  - implements a design algorithm in high-level language constructs
- RTL
  - describes the flow of data between registers and how a design processes that data
- Gate-Level
  - describes the logic gates and the connections between logic gates in a design
- Switch-Level
  - describes the transistors and storage nodes in a device and the connections between them



# Describing Components

---

```
module module_name port_list ;  
    // declarations  
    // statements  
endmodule
```

```
module and2 (o1, i1, i2);  
    input i1, i2;  
    output o1;  
    assign o1 = i1 & i2;  
endmodule
```





# Verilog Logic System

---

- 4 value logic system
  - 0 zero, false
  - 1 one, true
  - X unknown, conflict
  - Z high-impedance, unconnected




# Verilog Data Types

---

- Nets
  - Physical Connection between two devices
  - **wire, ...**
- Registers
  - Implicit Storage
  - Do not Imply Hardware Memory Elements
  - **reg, integer** (32 bit reg)

# Correct Port Connection

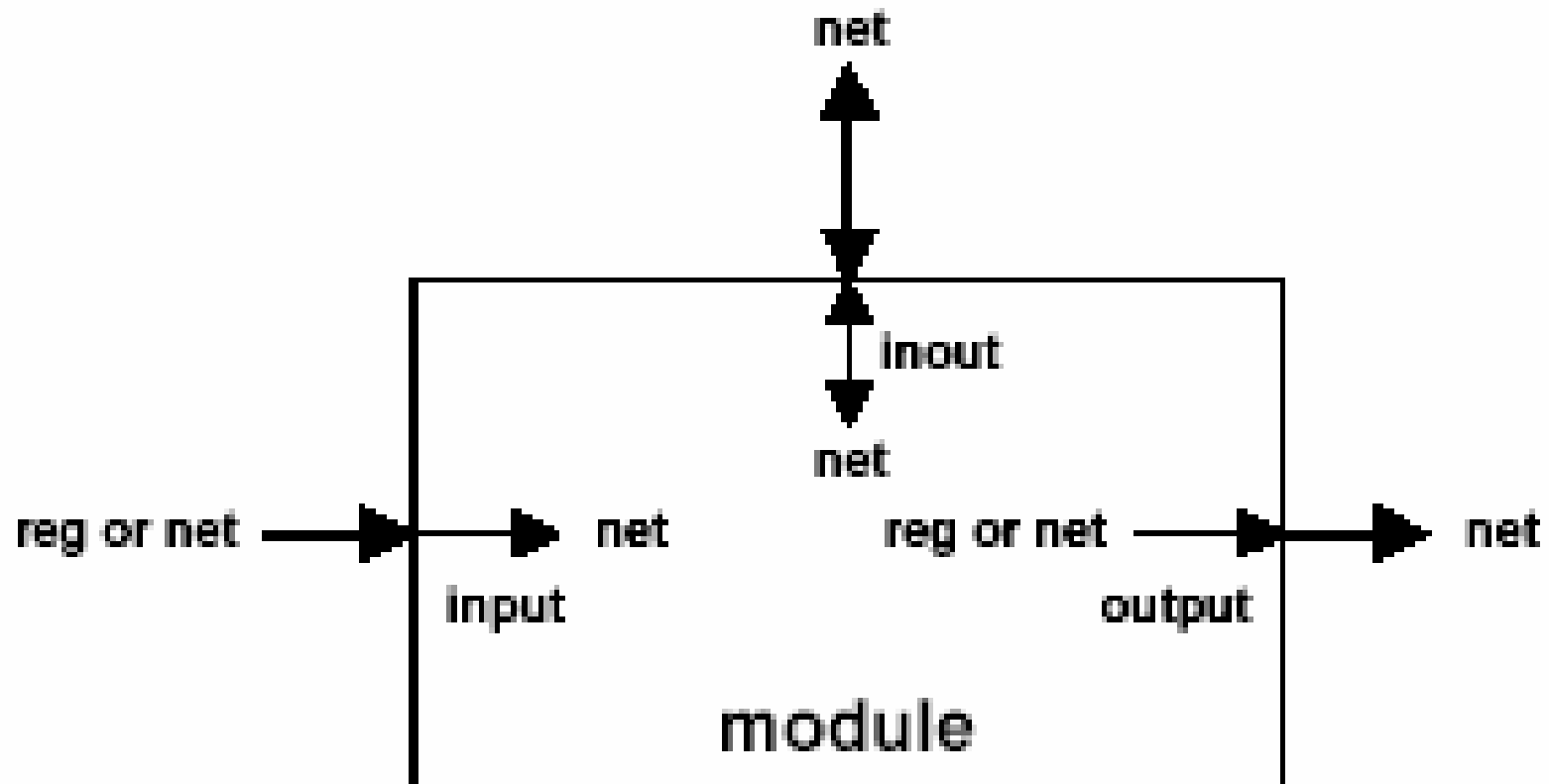



# Variable Declaration

---

```
wire range list_of_nets ;  
    wire w1, w2;  
    wire [7:0] w3;  
reg range list_of_registers ;  
    reg [0:11] r2, r3;  
integer list_of_integers ;  
    integer i1, i2;
```



# Port Modes

---

```
input range inpt_list ;  
output range inpt_list ;  
inout range inpt_list ;  
    input a, b;  
    output [7:0] c;
```

Note: ports are always considered as net,  
unless declared elsewhere as **reg**  
(only for output ports)



# Switch-Level Modeling

---

- MOS Switches:
  - nmos
  - pmos
- Bidirectional Pass Switches
  - tranif0
  - tranif1



## Example: CMOS Inverter

---

```
module cmos_inv (o1, i1);  
    input i1;  
    output o1;  
    supply1 vcc;  
    supply0 gnd;  
    pmos p1(o1, vcc, i1);  
    nmos n1(o1, gnd, i1);  
endmodule
```



# Gate-Level Modeling

---

- Primitive Gates
  - and, nand, or, nor, xor, xnor
  - GateType delay name (out, in1, ...);
- Buffer and Not
  - buf, not
  - GateType delay name (out, in);
- Tri-state Gates
  - bufif0, bufif1, notif0, notif1
  - GateType delay name (out, in, en);





# Gate Delays

---


- 1 delay
  - #(delay)
- 2 delay
  - #(rise\_delay, fall\_delay)
- 3 delay
  - #(rise\_delay, fall\_delay, off\_delay)
- Delay Elements
  - min:typical:max


 
# Example: Full Adder

---

```
module fa (co, s, a, b, ci);  
    input a, b, ci;  
    output co, s;  
    wire w1, w2, w3;  
  
    xor #(10) x1(s, a, b, ci);  
    and #(5, 4) a1(w1, a, b);  
    and #(5, 4) a2(w2, a, ci);  
    and #(5, 4) a3(w3, ci, b);  
    or #(5:6:7) o1(co, w1, w2, w3);  
endmodule
```



# Continuous Assignment

---

## Modeling Combinational Circuits

**assign** delay net\_var = expression ;

```
assign #10 co = a&b | a&ci | b&ci;
```

```
assign #12 s = a^b^ci;
```



# Operators

---

- Arithmetic
- Relational
- Bit-wise
- Logical
- Conditional
- Shift
- Reduction
- Concatenation
- Replication



# Bit-wise Operators

---

- $\sim$  NOT
- $\&$  AND
- $|$  OR
- $\wedge$  XOR
- $\sim \wedge$  or  $\wedge \sim$  XNOR



# Arithmetic Operators

---

- + Addition (unary and binary)
- - Subtraction (unary and binary)
- \* Multiplication
- / Division
- % Modulus

assign a = b + c ;



# Number Representation

---

- n'Fddd
  - n: length (default is 32)
  - F: base format
    - b Binary
    - o Octal
    - h hexadecimal
    - d Decimal (default)
  - ddd: legal digits for the base specified



# Number Examples

---

- 100 // decimal
- 8'b1000\_0110 // 8 bit binary
- 12'hF55 // 12 bit hex
- -4'd13 // 4 bit decimal
- 16'h1FFx // 16 bit hex with  
// 4 lsb unknown bits
- 'o34 // 32 bit octal





# Shift Operators

---

- <<      Shift Left
- >>      Shift Right

assign a = b << 2;

assign c = d >> 1;



# Conditional Operator

---

- `cond ? true_result : false_result`

`assign z = sel ? a : b ;`



# Reduction Operators

---

- $\&$  Reduction AND
- $|$  Reduction OR
- $\sim\&$  Reduction NAND
- $\sim|$  Reduction NOR
- $\wedge$  Reduction XOR
- $\sim\wedge$  or  $\wedge\sim$  Reduction XNOR



## Example: Parity Check

---

```
module parity_check(a, z);  
    input [7:0]  a;  
    output z;  
  
    assign z = ^a;    // reduction xor  
endmodule
```



# Concatenation Operator

---

- { } concatenation

assign {a, b} = c;

assign z = {2'b10, d};



## Example: Adder

---

```
module adder (co, s, a, b, ci);  
    input [7:0] a,b;  
    output [7:0] s;  
    input ci; output co;  
  
    assign {co, s} = a + b + ci;  
  
endmodule
```



# Replication Operator

---

- $\{n\{\text{item}\}\}$  replicate item n times

```
assign x = {4{4'h0}};
```

```
// assign x = 16'h0000;
```

```
assign z = {2{a}, 3{b}};
```

```
// assign z = {a, a, b, b, b};
```



# Relational Operators

---

- < less than
  - <= less than or equal
  - > greater than
  - >= greater than or equal
  - == equal
  - != not equal
- 
- Note: return value of these operators can be 0 or 1 or x





# Case Equality Operators

---

- `===` equal
- `!==` not equal

Return value of these operators can be only 0 or 1 (bit-by-bit comparison)



# Logical Operators

---

- `&&`                      logical AND
- `||`                        logical OR
- `!`                         logical NOT



## Example: Comparator

---


```
module comp (eq_o,lt_o,gt_o,a,b,eq_i,lt_i,gt_i);  
    parameter n = 4;  
    input [n-1:0] a, b;  
    output eq_o, lt_o, gt_o;  
    input eq_i, lt_i, gt_i;  
  
    assign eq_o = (a == b) && eq_i;  
    assign lt_o = (a < b) || ((a == b) && lt_i);  
    assign gt_o = (a > b) || ((a == b) && gt_i);  
endmodule
```



# Operator Precedence

---

- [] // bit select
- () // parentheses
- ! ~ // not
- & | ~& ~| ^ ^~ ~^  
// reduction
- + - //unary
- { } // concatenation
- {n{}} // replication
- \* / % // arithmetic
- + - // binary
- << >> // shift
- < <= > >= // relational
- == != // equality
- === !== // equality
- & // bit-wise
- ^ ~^ ^~ // bit-wise
- | // bit-wise
- && // logical
- || // logical
- ?: // conditional

 

# Structural Modeling

---

```
module Mux4x1 (z, a, s);  
    output z;  
    input [3:0] a;  
    input [1:0] s;  
    wire w1, w2;  
    Mux2x1 m1(w1, a[1:0], s[0]);  
    Mux2x1 m2(w2, a[3:2], s[0]);  
    Mux2x1 m3(z, {w2,w1}, s[1]);  
endmodule
```



# Always Block

---

always executes the statements sequentially from beginning to end of block until simulation terminates.

```
always event_control  
begin  
    // statements  
end
```



# Procedural Assignment

---

- Blocking Assignment
  - `delay reg = delay expression;`
- Non-Blocking (RTL) Assignment
  - `delay reg <= delay expression;`



# Blocking Assignment Example

---

```
always #10 clk = ~clk;
```

```
always begin
```

```
    a = 0;
```

```
    b = 1;
```

```
    #5 a = 1;
```

```
    b = x;
```

```
    c = #2 a;
```

```
end
```





# RTL Assignment Example

---

```
// swap every 100 time unit  
always begin  
    #100  
    a <= b;  
    b <= a;  
end
```



# Initial Block

---

begins execution of statements sequentially from the beginning of simulation and when reaches the last statement, terminates.

**initial**

**begin**

// statements

**end**



# Initial Block Example

---

```
initial a = 0;  
initial begin  
    a = 1;  
    b = 1;  
    b = 0;  
    #10 a = 0;  
    #15 b = 1;  
end
```



# If Statement

---


```
if (expression) begin
    // statements
end
else if (expression) begin
    // statements
end
// more else if blocks
else begin
    // statements
end
```


 
# Example: Multiplexer

---

```
module Mux2x1 (z, a, s);  
    output z;  
    input s;  
    input [1:0] a;  
    reg z;  
    always @(a or s)  
    begin  
        if (s == 0) z = a[0];  
        else z = a[1];  
    end  
endmodule
```



# Event Control

---

- @( edge\_control variable or ...)

always @(en) ...

always @(en or rst) ...

always @(**posedge** clk) ...

always @(**negedge** clk) ...



# Example: D-Latch

---

```
module d_latch (clk, q, q_bar, d);  
    input clk, d;  
    output q, q_bar;  
    reg q, q_bar;  
    always @(clk or d) begin  
        if (clk) begin  
            q <= d;  
            q_bar <= ~d;  
        end  
    end  
end  
endmodule
```



## Example: D-FF

---

```
module d_FF (clk, q, q_bar, d);  
    input clk, d;  
    output q, q_bar;  
    reg q, q_bar;  
    always @(posedge clk) begin  
        q <= d;  
        q_bar <= ~d;  
    end  
endmodule
```





# Case Statement

---

```
case (expression)
  chioce1:
    begin
      // statements
    end
  // more choices comes here
  default:
    begin
      // statements
    end
endcase
```



# Example: Moore 011 detector

---

```
module moore_011 (clk, x, z);  
    input clk, x;  
    output z; reg z;  
    reg[1:0] next, current;  
    parameter [1:0] reset = 2'b00;  
    parameter [1:0] got0 = 2'b01;  
    parameter [1:0] got01 = 2'b10;  
    parameter [1:0] got011 = 2'b11;  
  
    initial begin  
        current = reset;  
        next = reset;  
        z = 0;  
    end
```



## Moore 011 detector (cont.)

---

```
always @(posedge clk) current = next;
always @(current)
    if (next == got011) z = 1;
    else z = 0;

always @(x or current) begin
    case (current)
        reset: if (x) next = reset; else next = got0;
        got0: if (x) next = got01; else next = got0;
        got01: if (x) next = got011; else next = got0;
        got011: if (x) next = reset; else next = got0;
    endcase
end
endmodule
```



# Example: Mealy 011 Detector

---

```
`define reset 2'b00
`define got0 2'b01
`define got01 2'b10
module mealy_011 (clk, x, z);
    input clk, x;
    output z; reg z;
    reg[1:0] next, current;

    initial begin
        current = `reset;
        next = `reset;
        z = 0;
    end
end
```



## Mealy 011 Detector (cont.)

---

```
always @(posedge clk) current = next;

always @(current or x) z = (current == `got01 && x) ? 1 : 0;

always @(x or current)
begin
    case (current)
        `reset: if (x) next = `reset; else next = `got0;
        `got0: if (x) next = `got01; else next = `got0;
        `got01: if (x) next = `reset; else next = `got0;
    endcase
end
endmodule
```



# Handling Don't Care in case

---

- casez
  - Treat Z as don't care
- casex
  - Treat Z and X as don't care
- Use ? to show don't care in a position



# Example: Instruction Decode

---

...

casez (IR)

8'b1???????: ...

8'b01???????: ...

...

endcase



## Example: casex

---

```
// r = 8'b01100110
mask = 8'bx0x0x0x0;
casex (r ^ mask)
8'b001100xx: ...
8'b1100xx00: ... // this choice is true!
8'b00xx0011: ...
8'bx001100: ...
endcase
```





# Loop Statements

---


- **forever**
  - continuously executes statements
- **repeat**
  - execute statements fixed number of times
- **while**
  - execute statements while condition is true
- **for**
  - is like c++ for statement


 
# Example: Multiplication

---

```
module mult(result, opa, opb);
    parameter size = 8, longsize = 16;
    input [size:1] opa, opb;
    output [longsize:1] result;
    reg [longsize:1] result;
    reg [longsize:1] shift_opa, shift_opb;
    always @(opa or opb) begin
        shift_opa = opa; shift_opb = opb; result = 0;
        repeat(size)
            begin
                if (shift_opb[1]) result = result + shift_opa;
                shift_opa = shift_opa <<1;
                shift_opb = shift_opb >>1;
            end
        end
    end
endmodule
```



## Example: Memory

---

```
reg [7:0] mem_array [0:1023];  
integer cnt;  
initial begin  
    for (cnt = 0; cnt < 1024; cnt = cnt+1)  
        mem_array[cnt] = 0;  
end
```



## Example: count 1's

---

```
always @(rega) begin
    count = 0;
    tempreg = rega;
    while (tempreg)
    begin
        if (tempreg[0]) count = count + 1;
        tempreg = tempreg >> 1;
    end
end
```



# Tasks

---

```
task task_name;  
    // declare inputs and outputs  
begin  
    // statements  
end  
endtask
```



# Example: Traffic Light

---

```
module traffic_lights;
    reg clock, red, amber, green;
    parameter on = 1, off = 0, red_tics = 350, amber_tics = 30,
    green_tics = 200;
    // initialize colors
    Initial begin red = off; amber = off; green = off; end
    // sequence to control the lights
    always begin
        red = on; // turn red light on
        light(red, red_tics); // and wait.
        green = on; // turn green light on
        light(green, green_tics); // and wait.
        amber = on; // turn amber light on
        light(amber, amber_tics); // and wait.
    end
end
```



## Traffic Light (cont.)

---

```
// wait for 'tics' positive edge clocks before turning 'color' light off
task light;
    output color;
    input [31:0] tics;
    begin
        repeat (tics)
            @(posedge clock);
            color = off; // turn light off
        end
    endtask
// waveform for the clock
always begin #100 clock = ~clock; end

endmodule // traffic_lights
```



 
# Function

---

```
function range_or_type func_name;  
    // declare input ports  
begin  
    // statements  
    func_name = result;  
end  
endfunction
```





# Function Rules

---

- Can not contain any event control
- Can not enable tasks
- Must contain at least one input parameter
- Must include an assignment to the function name (return value)



# Example: Factorial

---

```
function [31:0] factorial;  
    input [3:0] operand;  
    reg [3:0] index;  
    begin  
        factorial = operand ? 1 : 0;  
        for (index = 2; index <= operand; index = index+1)  
            factorial = index * factorial;  
    end  
endfunction  
...  
assign res = n * factorial(n);
```



# System Tasks and Functions

---

- `$display("format_string", par1, ...);`
- `$monitor("format_string", par1, ...);`
- `$time`
- `$reset`
- `$halt`
- `$random`



# Compiler Directives

---

- ``define`
- ``timescale time_unit/time_preceision`
- ``include "file_name"`